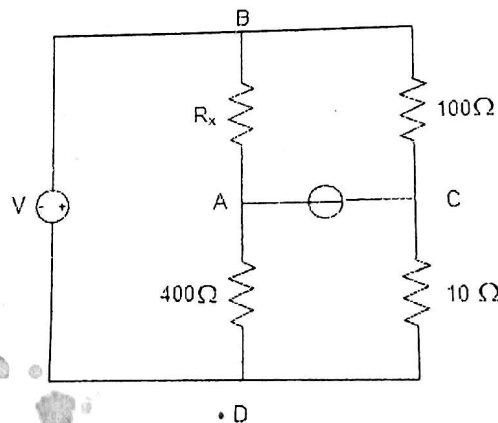


1. Fill in the blank spaces below. (Write the answers in your answer sheet).

- I. The symbol for **admittance** is _____.
- II. The symbol for **susceptance** is _____.
- III. The reciprocal of **reactance** is called _____.
- IV. The reciprocal of **resistance** is called Conductance.
- V. If a circuit's total **impedance increases** while the source voltage is held constant, the circuit's total **current** _____.
- VI. In a **series** connection, is the total equivalent **conductance** greater, equal to or less than the individual **conductances**?

2. Find the value of the unknown resistance in the bridge circuit illustrated below;



3. Perform the following operation and express the final answer in polar form.

$$5 \angle 30^\circ + 8 \angle -30^\circ$$

4. A series AC circuit exhibits a total impedance of $2.5k$, with a phase shift of 30 degrees between voltage and current. Drawn in an impedance triangle, it looks like this:

