

GET 209 (part II)

Course Outline

- DC/AC Bridges: Resistance, Capacitance and Inductance Measurement
- Transducers
- Single phase circuits
- Complex J - Notation
- AC circuits
- Impedance
- Admittance
- Susceptance

Texts

• J. A. Svoboda and R. C. Dorf, Introduction to Electric Circuits, 9th Edition, Wiley

— William H. Hayt, Jack E. Kemmerly and Steven M. Durbin, Engineering Circuit Analysis

~ G. K. Alexander and Matthew N. O. Sadiku, Fundamentals of Electric Circuits

~ B. L. Theraja and A. K. Theraja, Electrics Technology

DC/AC Bridges


Bridge Circuits are used very commonly as a variable conversion element in measurement systems and produce an output in the form of a voltage level that changes as the meas. physical quantity changes. They provide an accurate method of measuring resistance, inductance and capacitance values, and enable the detection of very small changes in these quantities about a nominal value. The use of resistance in measurement system technology because so many transducers measuring physical quantities have an output that is expressed as a change in resistance, inductance or capacitance.

Resistance Measurement with Wheatstone Bridge

While ohmmeters are designed to measure resistance in low, mid or high range, a Wheatstone bridge is used to measure resistance in the mid range, say, between 1Ω and $1M\Omega$. Very low values of resistances are measured with a milliohmmeter while very high values are measured with a megger tester.

Wheatstone Bridge

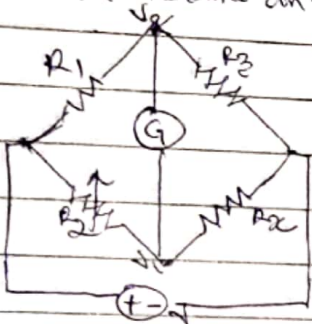The Wheatstone bridge (or resistance bridge) circuit is used in a number of applications. Here we will use it to measure an unknown resistance.



$$V_1 = \frac{R_2}{R_1 + R_2} V = V_2 = \frac{R_x}{R_3 + R_x} V$$

$$\frac{R_2}{R_1 + R_2} = \frac{R_x}{R_3 + R_x}$$

$$R_2 R_3 = R_1 R_x$$


$$R_x = \frac{R_3 R_2}{R_1}$$

If $R_1 = R_3$ & R_2 is adjusted until no current flows through the galvanometer, then $R_x = R_2$.

Example 01. Consider a balanced Wheatstone bridge with $R_1 = 500\Omega$ and $R_2 = 200\Omega$. Def. the unknown resistance when $R_3 = 125\Omega$.

Example 02. A Wheatstone bridge has $R_1 = R_3 = 1K\Omega$. R_2 is adjusted until no current flows through the galvanometer. At that point, $R_4 = 3.2K\Omega$. What is the value of the unknown resistance? **Ans** $= 3.2K\Omega$

Unbalanced Wheatstone Bridge

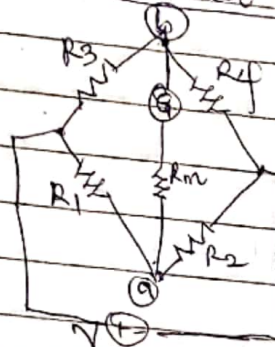

To find the current through the galvanometer when the Wheatstone bridge is unbalanced?

Find the Thevenin equivalent V_{th} & R_{th} with respect to the galvanometer terminals. If R_m is the resistance of the galvanometer, the current through it under the unbalanced condition is:


$$I = \frac{V_{th}}{R_{th} + R_m}$$

$$\text{where } R_{th} = (R_1 \parallel R_2) + (R_3 \parallel R_4)$$

$$V_{th} = V_a - V_b$$

$$V_a = \frac{R_2}{R_1 + R_2} V \quad \text{and} \quad V_b = \frac{R_4}{R_3 + R_4} V$$

Example 03.

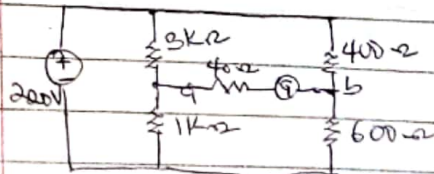

The circuit represents an unbalanced bridge. If the galvanometer has a resistance of 40Ω , find the current through the galvanometer.


$\frac{R_1}{R_2} = \frac{L_1}{L_2}$ or $\frac{L_1}{L_2} = \frac{R_2}{R_1}$
 $\frac{R_1}{R_2} = \frac{L_1}{L_2}$ or $\frac{L_1}{L_2} = \frac{R_2}{R_1}$
 Used for measurement of inductance over a wide range from few micro to several henrys.
 It is a modified Maxwell-Wien bridge with an unknown inductance is measured in terms of known capacitance and resistance.
 Anderson Bridge

AC BRIDGES

- Like Measurement of resistance by a d.c. Wheatstone bridge, Inductance and Capacitance can also be measured in a similar way.
- The d.c. Signal changer to an AC signal and a galvanometer is replaced by a Vibrating galvanometer.

Condition of Balance

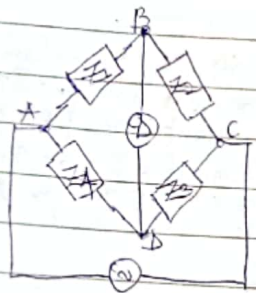There must be a balance of impedance in magnitude and phase.



When the bridge is balanced, the potential at node B is equal to the potential at node D.

Thus
$$\frac{Z_3}{Z_1 Z_2} = \frac{Z_4}{Z_1 Z_2}$$

$$\boxed{\frac{Z_1}{Z_2} = \frac{Z_4}{Z_3}}$$

Now for an AC network

$$Z_1 = Z_1 \angle \phi_1$$

$$Z_2 = Z_2 \angle \phi_2$$

$$Z_3 = Z_3 \angle \phi_3$$

$$Z_4 = Z_4 \angle \phi_4$$

Hence

$$Z_1 \angle \phi_1 \times Z_3 \angle \phi_3 = Z_2 \angle \phi_2 \times Z_4 \angle \phi_4$$

$$Z_1 Z_3 \angle \phi_1 + \phi_3 = Z_2 Z_4 \angle \phi_2 + \phi_4$$


Thus for a balanced impedance bridge

i. $Z_1 Z_3 = Z_2 Z_4$

ii. $\phi_1 + \phi_3 = \phi_2 + \phi_4$

Inductance Measurement

(a) Maxwell's Inductance Bridge

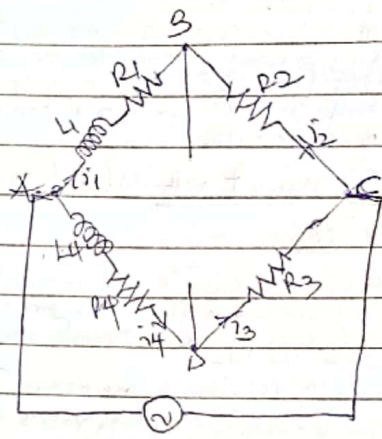

Let Z_1 be an unknown impedance

Z_3 can be impedance of equal phase which can be used in the adjacent arm, such that $\phi_1 = \phi_3$ or $\phi_2 = \phi_4$.

* If BC and DC have zero phase angle i.e. pure resistors, such network is called Maxwell's AC bridge or $\frac{1}{4}$ bridge

* Otherwise, if an impedance with negative phase shift (phase angle) is used (capacitor) in the adjacent arm, such that $\phi_1 + \phi_3 = 0$, such is known as Maxwell-Wien bridge or $\frac{1}{2}$ bridge

$$Z_1 = R_1 + jX_1 = R_1 + j\omega L_1 \quad \text{Unknown}$$

$$Z_4 = R_4 + jX_4 = R_4 + j\omega L_4 \quad \text{Known}$$

R_2 & $R_3 \Rightarrow$ Known pure resistors

$X = \omega L$ or ωC

The bridge is balanced by varying L_4 and R_2 or R_3 . Since R_2 & R_3 are constant while one of R_1 & L_1 can be varied

AC Bridges

Like Measurement of resistance by a dc
 Wheatstone bridge, inductance and capacitance can also be measured in a similar way.

$$1. Z_1 Z_3 = Z_2 Z_4$$

$$2. C_1 + C_3 = C_2 + C_4$$

then, $Z_1 Z_3 = Z_2 Z_4$

$$(R_1 + j\omega L_1) R_3 = (R_2 + j\omega L_2) R_4$$

$$R_1 R_3 + j\omega L_1 R_3 = R_2 R_4 + j\omega L_2 R_4$$

Equating the real & imaginary

$$\frac{R_1}{R_2} = \frac{R_4}{R_3} \quad \text{or} \quad \frac{L_1}{L_2} = \frac{R_2}{R_3}$$

$$\text{then } L_1 = \frac{R_2 R_4}{R_3} \quad \text{or} \quad L_2 = L_1 \frac{R_1}{R_4} \quad \text{or} \quad \frac{L_1}{R_1} = \frac{L_2}{R_4}$$

Example In the fig above, R_4 and L_1 if

$$R_1 = 32.7 \Omega, R_2 = \text{Unknown}, R_3 = R_4 = 100 \Omega$$

$$R \text{ (in series with } R_4) = 136 \Omega, L_1 = 47.8 \text{ mH. Balance}$$

can be obtained by L_1 & R_4 and R_1 & L_1 .

Soln


$$R_1 R_3 = R_2 (R_4 + R_2)$$

$$32.7 \times 100 = 100 (136 + R_2)$$

$$R_4 = 30.34 \Omega$$

$$L_1 / L_2 = R_2 / R_3 \quad \therefore L_1 = 47.8 \text{ mH}$$

② Maxwell-Wien Bridge or AC Bridge

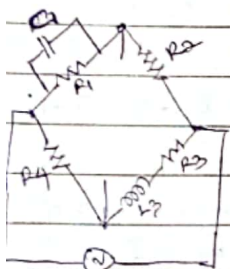

$$\frac{1}{Z_1} = \frac{1}{R_1} + \frac{1}{j\omega C}$$

$$= \frac{1}{R_1} + j\frac{1}{\omega C}$$

$$\frac{1}{Z_2} = \frac{1}{R_2} + j\omega C$$

$$Z_1 = \frac{R_1}{1 + j\omega C R_1}$$

$$Z_2 = R_2$$

$$Z_3 = R_3 + j\omega L_3$$

$$Z_4 = R_4$$

③ Balance $Z_1 Z_3 = Z_2 Z_4$

$$\frac{R_1 (R_3 + j\omega L_3)}{1 + j\omega C R_1} = R_2 R_4$$

$$R_1 R_3 + j\omega L_3 R_1 = R_2 R_4 + j\omega C R_1 R_2 R_4$$

$$R_1 R_3 = R_2 R_4$$

and

$$L_3 R_1 = C R_1 R_2 R_4$$

Example

Given a Maxwell-Wien bridge with $R_1 = 1000 \Omega$, $C = 0.5 \mu\text{F}$, $R_2 = 600 \Omega$ and $R_4 = 400 \Omega$.

Def. R_3 and L_3 @ Balance

Soln


$$R_3 = \frac{R_2 R_4}{R_1} = \frac{600 \times 400}{1000} = 240 \Omega$$

$$L_3 = C R_2 R_4 = 0.5 \times 10^{-6} \times 600 \times 400 = 0.12 \text{ mH}$$

Anderson Bridge

Used for measuring inductance over a wide range from few micro Henrys to henrys.

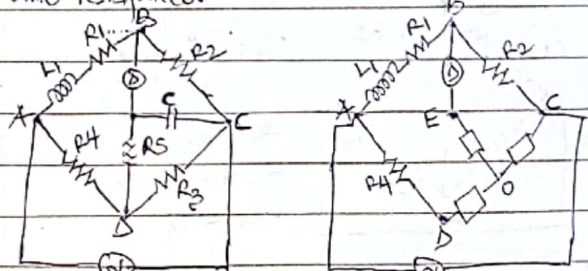It is a modified Maxwell-Wien bridge where unknown inductance is measured in terms of known capacitance and resistance.



$$Z_{op} = \frac{R_3 R_5}{(R_3 + R_5) + j\omega C}$$

$$Z_{oc} = \frac{R_3 (j\omega C)}{(R_3 + R_5) + j\omega C}$$

$$Z_{oe} = \frac{R_5 (j\omega C)}{(R_3 + R_5) + j\omega C}$$

$$\text{then } Z_1 = R_1 + j\omega L_1$$

$$Z_2 = R_2$$

$$Z_3 = Z_{oc}$$

$$Z_4 = R_4 + Z_{oe}$$

For balance, $Z_1 Z_3 = Z_2 Z_4$

$$(R_1 + j\omega L_1) Z_{oc} = R_2 (R_4 + Z_{oe})$$

$$(R_1 + j\omega L_1) \frac{R_3 (j\omega C)}{(R_3 + R_5) + j\omega C} = R_2 \left[R_4 + \frac{R_5 (j\omega C)}{(R_3 + R_5) + j\omega C} \right]$$

$$R_1 R_3 R_4 + R_2 R_4 R_5 - j R_2 R_4 \frac{R_3 R_5}{(R_3 + R_5) + j\omega C} = j \frac{R_1 R_3 + R_5 L_1}{\omega C}$$

Equating the real & imaginary

$$-j R_2 R_4 \frac{R_3 R_5}{\omega C} = -j \frac{R_1 R_3}{\omega C}$$

$$R_1 = \frac{R_2 R_4}{R_3}$$

$$R_2 R_3 R_4 + R_2 R_4 R_5 + R_2 R_3 R_5 = \frac{R_3 L_1}{C}$$

$$L_1 = C R_2 \left[R_4 + R_5 + \frac{R_4 R_5}{R_3} \right]$$

Example

In the Anderson bridge above let R_1 & L_1 be unknown

$$R_2 = 1000 \Omega$$

$$R_4 = 2000 \Omega$$

$$R_3 = 2000 \Omega$$

$$C = 1 \mu\text{F}$$

$$R_5 = 200 \Omega$$

Soln


$$R_1 = \frac{R_2 R_4}{R_3} = \frac{1000 \times 2000}{2000} = 1000 \Omega$$

$$L_1 = C R_2 \left(R_4 + R_5 + \frac{R_4 R_5}{R_3} \right) = 24 \text{ mH}$$

Measurement of capacitance can be obtained by using the Schering Bridge

Hay's Bridge

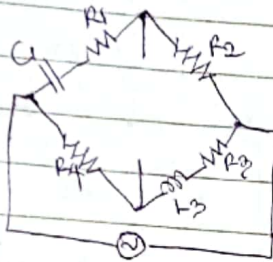It is also a modification of Maxwell-Wien bridge and used when the phase angle of the inductive impedance $\phi_m = \tan^{-1}(\frac{WL}{R})$ is large.



$$\begin{aligned} Z_1 &= R_1 + \frac{1}{j\omega C_1} \\ &= R_1 - j\frac{1}{\omega C_1} \\ Z_2 &= R_2 \\ Z_3 &= R_3 + j\omega L_3 \\ Z_4 &= R_4 \end{aligned}$$

Balance Condition: $Z_1 Z_3 = Z_2 Z_4$

$$(R_1 - j\frac{1}{\omega C_1})(R_3 + j\omega L_3) = R_2 R_4$$

$$R_1 R_3 + j\omega L_3 R_1 - j\frac{R_3}{\omega C_1} + \frac{L_3}{C_1} = R_2 R_4$$

Separate the real and the imaginary

$$R_1 R_3 + \frac{L_3}{C_1} = R_2 R_4 \quad \text{--- (1)}$$

$$\omega L_3 - \frac{R_3}{\omega C_1} = 0 \quad \text{--- (2)}$$

Simplify the two equations simultaneously

$$L_3 = \frac{C_1 R_2 R_4}{1 + \omega^2 R_1^2 C_1^2} \quad \text{and} \quad R_3 = \frac{\omega^2 C_1^2 R_1 R_2 R_4}{1 + \omega^2 R_1^2 C_1^2}$$

Example Solve given that $f = 50 \text{ Hz}$

R_1 & L_1 are unknown, $R_2 = 16800 \Omega$, $R_3 = 1000 \Omega$, $R_4 = 883 \Omega$, $C = 0.38 \mu\text{F}$. Find R_1 & L_1 for an Hay's bridge.

Soln $\omega = 2\pi f = 2 \times 3.14 \times 50 = 314.29 \text{ rad/s}$


$\omega^2 = 314.29^2 = 98721$

Apply the equations above

$R_1 = 210 \Omega$

$L_1 = 6.38 \text{ H}$

Owen Bridge

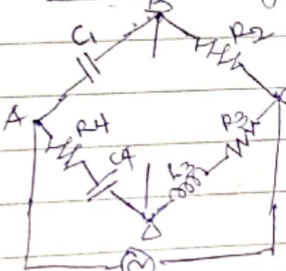

Balance Condition: $Z_1 Z_3 = Z_2 Z_4$

$$\begin{aligned} Z_1 &= -j/\omega C_1 \\ Z_2 &= R_2 \\ Z_3 &= R_3 + j\omega L_3 \\ Z_4 &= R_4 - j/\omega C_4 \end{aligned}$$

$$-j \frac{1}{\omega C_1} (R_3 + j\omega L_3) = R_2 \left[R_4 - \frac{j}{\omega C_4} \right]$$

Separate the real and imaginary

$$R_3 = \frac{R_2 R_4}{C_4}$$

$$L_3 = \frac{C_2 R_2 R_4}{C_4}$$


This bridge is unaffected by the frequency of variation and waveform.

Exercise

1. An a.c. bridge is arranged as follows: The arms AB and BC consist of non-inductive resistance of 100Ω , the arms BE and CD of non-inductive variable resistance, the arm EC of a capacitor of $1 \mu\text{F}$ capacitance, the arm DA of an inductive resistance. The a.c. source is connected to A and C and the telephone receiver to E and D. A balance is obtained when the resistance of the arms CD and BE are 50Ω and 2500Ω respectively.

Calculate the resistance and the inductance of the arm DA. What would be the effect of harmonics on the waveform of the alternating current source. [50Ω ; 0.25 H]

2.

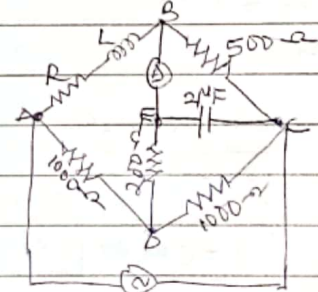


Determine the values of unknown resistance R and inductance L [500Ω ; 1.5 H]

$R_2 = \frac{R_1 C_1}{C_2}$
 Separating the real and imaginary parts
 It is also a modification of Maxwell-Wien bridge
 The phase angle of the capacitor impedance
 $\phi_m = \tan^{-1} \left(\frac{R}{X_C} \right)$ is large.

Capacitance Bridges

Measurement of capacitance can be obtained using De Sauty bridge Method and Schering bridge Method.

De Sauty Bridge

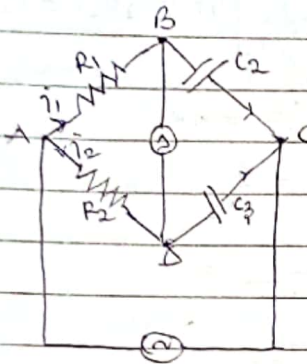

Given that C_2 is unknown

$C_3 \Rightarrow$ Known

R_1 and R_2 are given

Balance is obtained by varying either R_1 or R_2 such that the potential @ B and D are equal

Then $i_1 R_1 = i_2 R_2$

$$\frac{-j}{\omega C_2} i_1 = \frac{-j}{\omega C_3} i_2$$

Equating the two equations

$$\frac{R_1}{R_2} = \frac{C_2}{C_3}$$


$$C_2 = C_3 \frac{R_1}{R_2}$$

It may be impossible to obtain perfect balance if the capacitors are not free of dielectric loss.

A perfect balance is only possible if air capacitors are used.

Schering Bridge

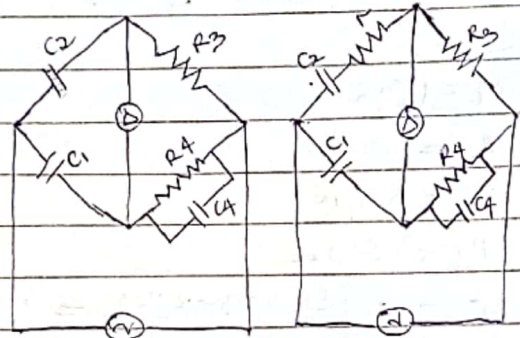Useful in measuring the capacitance and dielectric loss of a capacitor. It works by comparing an imperfect capacitor C_2 in terms of a loss free capacitor C_1 .



The imperfect capacitor C_2 can be represented by its equivalent loss-free capacitor C_2 in series with resistance r

$$Z_1 = r - \frac{j}{\omega C_1}$$

$$Z_2 = r - \frac{j}{\omega C_2}$$

$$Z_3 = R_3$$

$$Z_4 = \frac{1}{(R_4 + j\omega C_4 R_4)} = \frac{R_4}{1 + j\omega C_4 R_4}$$

The balance condition is that, $Z_1 Z_3 = Z_2 Z_4$

$$\frac{-j R_3}{\omega C_1} = \left(r - \frac{j}{\omega C_2} \right) \left(\frac{R_4}{1 + j\omega C_4 R_4} \right)$$

$$\frac{-j R_3}{\omega C_1} (1 + j\omega C_4 R_4) = R_4 \left[r - \frac{j}{\omega C_2} \right]$$

Separating the real and imaginary parts

$$C_2 = C_1 \left\{ \frac{R_4}{R_3} \right\}$$

$$r = R_3 \left\{ \frac{C_4}{C_1} \right\}$$

Example: A loss capacitor is tested with a Schering bridge circuit. A balance is obtained with the capacitor under test in one arm, the succeeding arms

Keep a non-inductive resistor of 100Ω , a non-reactive resistor of 300Ω in parallel with a pure capacitor of $0.5\mu F$ and a standard capacitor of $100\mu F$. The supply frequency is 50Hz . Calculate the series capacitance and the equivalent resistance.

Soln

$$C_1 = 100\mu F$$

$$R_3 = 100\Omega$$

$$C_4 = 0.5\mu F$$


$$R_4 = 300\Omega$$

$$C_2 \approx C_1 \left\{ \frac{R_4}{R_3} \right\} = 100 \times \frac{300}{100} = 336.8\mu F$$

$$r \approx R_3 \left\{ \frac{C_4}{C_1} \right\} = 100 \left\{ \frac{0.5 \times 10^{-6}}{100 \times 10^{-6}} \right\} =$$

Wien Series Bridge / Wien Parallel Bridge
 They are simple radio bridges used for audio-frequency measurement of capacitors over a wide range.


(a) Wien Series Bridge

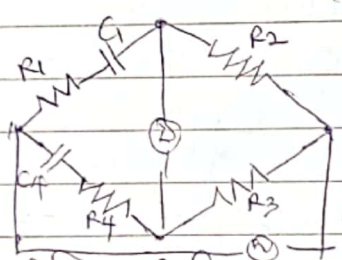

After the bridge is balance

$$R_1 = \frac{R_2 R_4}{R_3} \quad \text{and} \quad C_1 = C_4 \left(\frac{R_3}{R_2} \right)$$

(b)

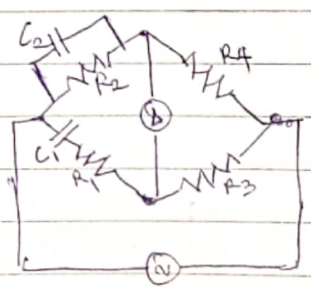

Wien parallel bridge can also be used to measure audio frequencies, though not as accurate as the normal frequency meter.

Condition of balance

$$R_4 \left\{ R_1 - \frac{j}{\omega C_1} \right\} = R_3 \left\{ \frac{R_2}{1 + j\omega C_2 R_2} \right\}$$

$$R_4 \left\{ R_1 - \frac{j}{\omega C_1} \right\} (1 + j\omega C_2 R_2) = R_2 R_3$$

Separate the real and imaginary terms

$$R_1 R_4 + R_2 R_4 \frac{C_2}{C_1} = R_2 R_3$$


$$\text{or } \frac{C_2}{C_1} = \frac{R_3}{R_4} = \frac{R_1}{R_2}$$

$$\text{and } \omega C_2 R_2 R_4 - \frac{R_4}{\omega C_1} = 0$$

$$\omega^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

Example

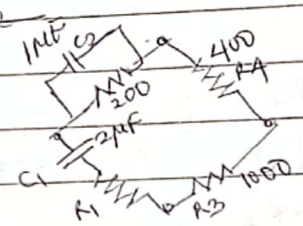

Def. R_1 and the supply frequency when the bridge is balanced.

Soln

$$\frac{C_2}{C_1} = \frac{R_3}{R_4} = \frac{R_1}{R_2}$$

$$\frac{2}{1} = \frac{1000}{4000} = \frac{R_1}{200}$$

$$R_1 = 200 \times 0.5 = 100\Omega$$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

$$= \frac{10^8}{2\pi \sqrt{100 \times 200 \times 1 \times 2}} = 796\text{ Hz}$$